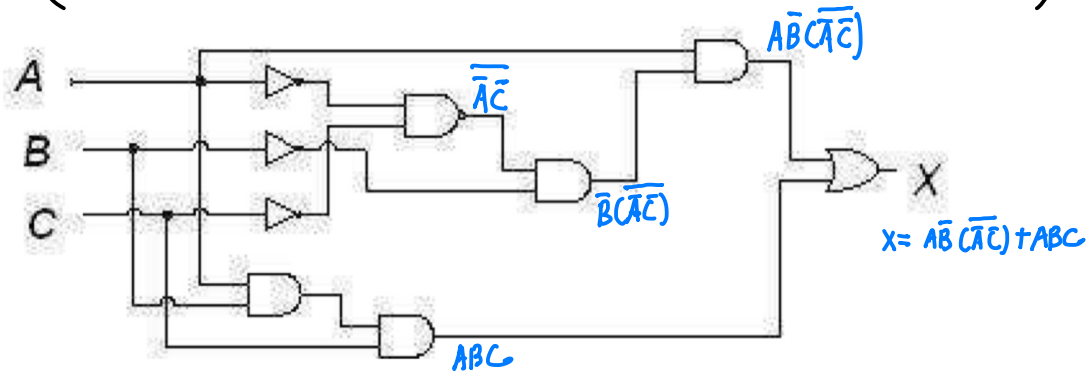


1) MUI RUI XIN  
2) YIAP WEI SHANZ

243UC247CT  
243UC247CV

1. (i) Identify the (Boolean expression) for the given logic diagram and obtain the (truth table)



1)(i)

$$X = \bar{A}\bar{B}(\bar{A}\bar{C}) + ABC$$


Inputs			✓ Output					
A	B	C	ABC	$\bar{A}\bar{C}$	$\bar{A}\bar{C}$	$\bar{B}(\bar{A}\bar{C})$	$\bar{A}\bar{B}(\bar{A}\bar{C})$	X
0	0	0	0	1	0	0	0	0
0	0	1	0	0	1	1	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	1	0	0	0	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	1	1	1	1
1	1	0	0	0	1	0	0	0
	1	1	1	0	1	0	0	1

- (ii) (Simplify) the identified expression using the Boolean rules, laws and theorems. Draw the truth table for the simplified Boolean expression. (Construct the circuit) only for the simplified expression and verify the (truth table) experimentally.


$$\begin{aligned}
 (ii) \quad X &= A\bar{B}(\bar{A}\bar{C}) + ABC \\
 &= A\bar{B}(\bar{A} + \bar{C}) + ABC \\
 &= A\bar{B}(A + C) + ABC \\
 &= A\bar{B}A + A\bar{B}C + ABC \\
 &= A\bar{B} + A(\bar{B}C + B) \\
 &= A\bar{B} + AC \\
 X &= A(\bar{B} + C)
 \end{aligned}$$

Inputs			Output		
A	B	C	$\bar{B}$	$\bar{B} + C$	X
0	0	0	1	1	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	0	1	1

$$X = A(\bar{B} + C)$$

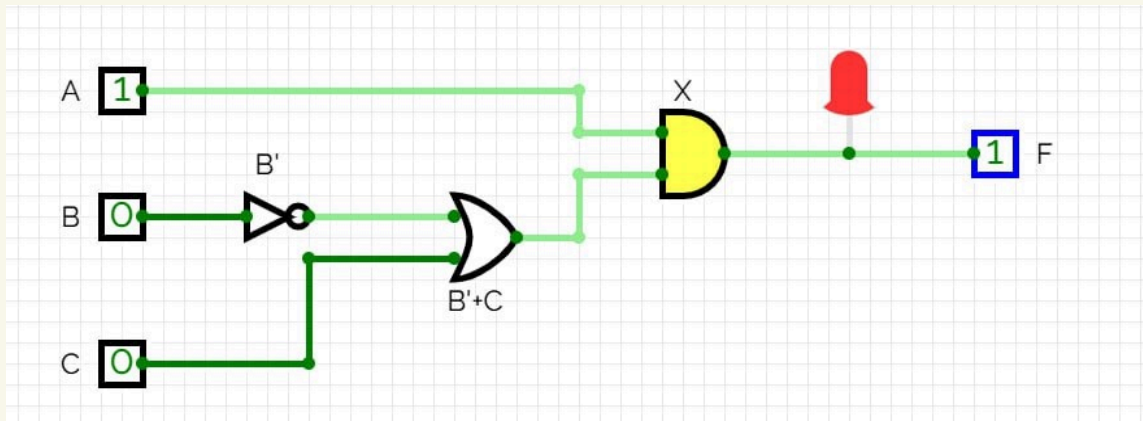

2. (i)

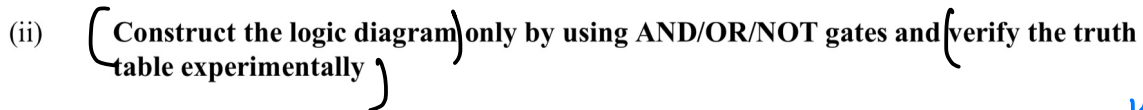

$$F = \left[ \left[ (CAB)'(CAB)' \right]' (AB)'(AB)' \right]' \left[ \left[ (CD)'(CD)' \right]' (CD)'(CD)' \right]' \right]'$$


2) (i)

$$\begin{aligned}
 F &= \left[ \left[ \left[ (AB)'(AB)' \right]' \left[ (AB)'(AB)' \right]' \right]' \left[ \left[ (CD)'(CD)' \right]' \left[ (CD)'(CD)' \right]' \right]' \right]' \\
 &= \left[ \left[ \left[ (AB)' \right]' \left[ (AB)' \right]' \right]' \left[ \left[ (CD)' \right]' \left[ (CD)' \right]' \right]' \right]' \\
 &= \left[ \left[ (AB)''(AB)'' \right]' \left[ (CD)''(CD)'' \right]' \right]' \\
 &= \left[ \left[ (AB)'' \right]' \left[ (CD)'' \right]' \right]' \\
 &= \left[ (AB)'(CD)' \right]' \\
 &= \left[ (AB)' \right]' + \left[ (CD)' \right]' \\
 &= (AB)'' + (CD)''
 \end{aligned}$$

$$F = AB + CD \quad (\text{SOP})$$


Input				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(ii)

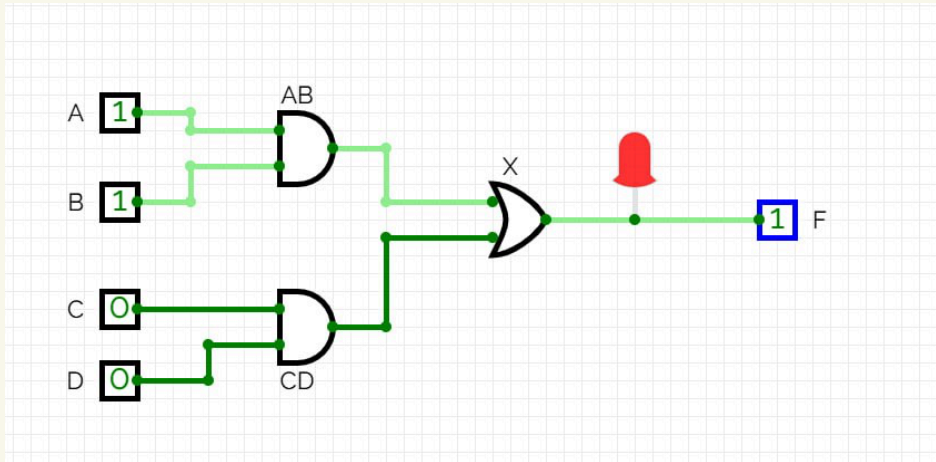

Input				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

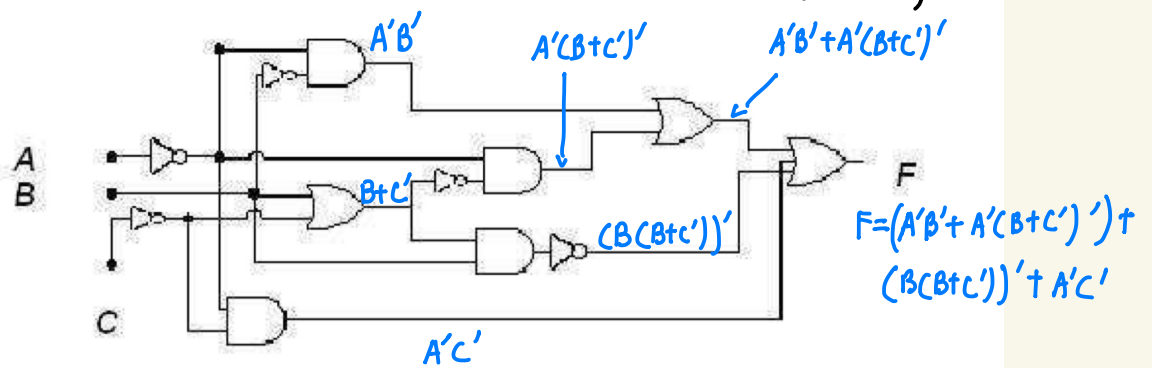3. (i) Identify the (Boolean expression) for the given logic diagram and obtain the (truth table.)



- (ii) (Simplify) the identified expression using the Boolean rules, laws and theorems. Draw the (truth table) for the simplified Boolean expression. (Construct the circuit) for the simplified expression.

3)(i)  $F = A'B' + A'(B+C')' + (B(B+C'))' + A'C'$

Inputs			Output
A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$\begin{aligned}
 (ii) \quad F &= A'B' + A'(B+C')' + (B(B+C'))' + A'C' \\
 &= A'B' + A'(B' \cdot C'') + (B' + (B+C'))' + A'C' \\
 &= A'B' + A'B'C + (B' + (B' + C')) + A'C' \\
 &= A'B' + A'B'C + (B' + B' + C) + A'C' \\
 &= A'B' + A'B'C + B' + B'C + A'C' \\
 &= B'(A' + A'C + 1 + C) + A'C' \\
 &= B'(1) + A'C'
 \end{aligned}$$

$$(B+C)' = B'C'$$


$$(BC)' = B' + C'$$

$$1+A=1$$


$$1(A)=A$$

$$F = A'C' + B'$$

Inputs			Output
A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

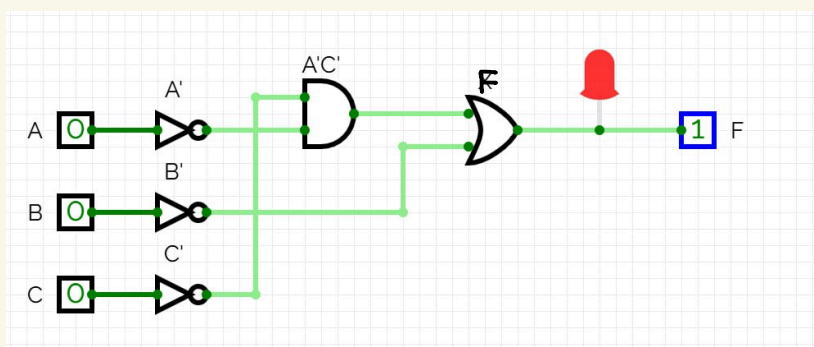

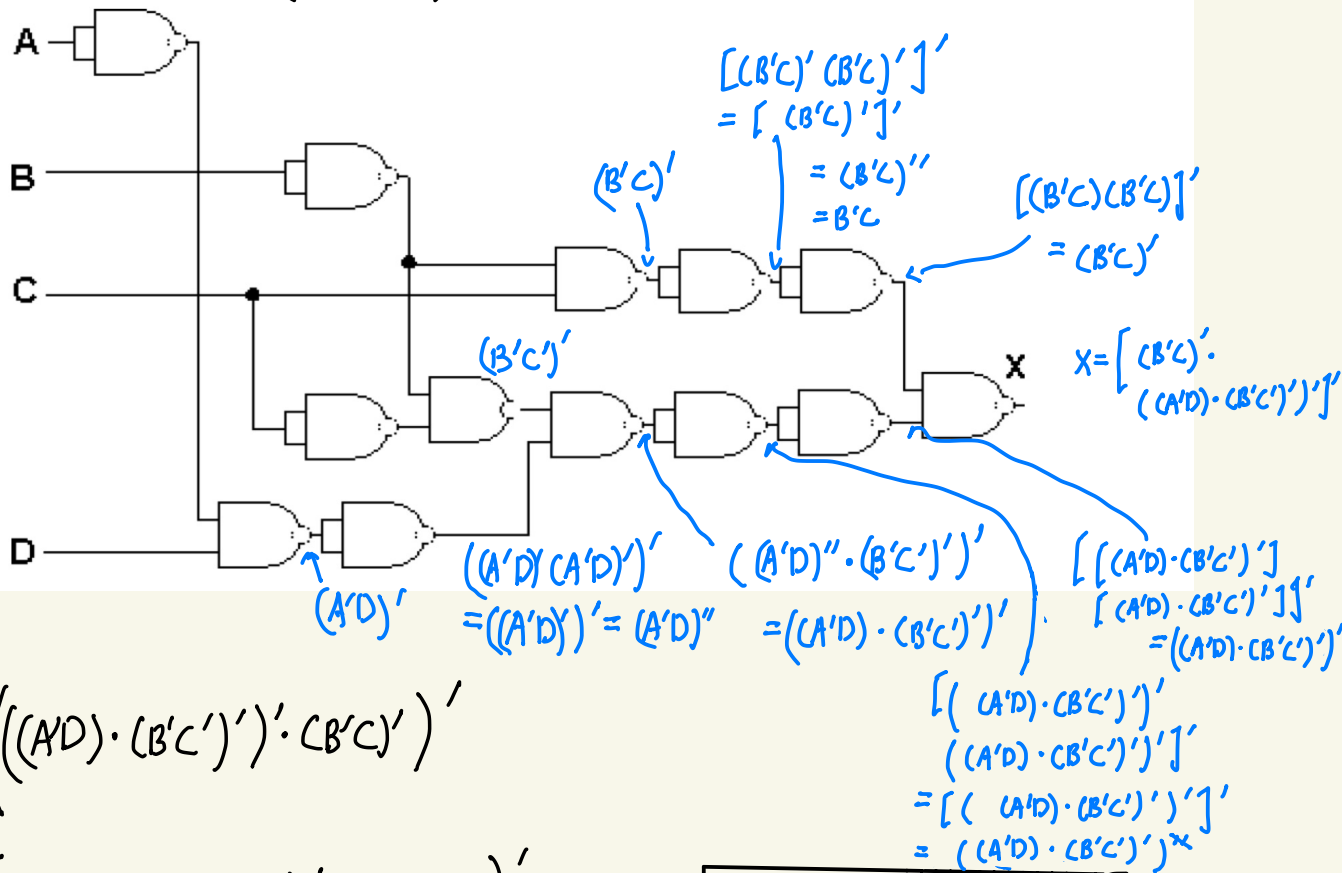4. (i) Obtain sum of products expression for the given NAND network and draw the truth table.  
(ii) Construct the logic diagram using AND/OR/NOT gates.



4)(i)  $F = ((A'D) \cdot (B'C')')' \cdot (B'C')'$

$$F = ((A'D) \cdot (B'' + C''))' \cdot (B'' + C')$$

$$= ((A'DB + A'DC)' \cdot (B + C'))'$$


$$= (A'DB + A'DC)'' + (B + C')'$$

$$= A'DB + A'DC + (B'C'')$$

$$= A'DB + A'DC + B'C$$


$$F = A'BD + A'CD + B'C \quad (\text{SOP})$$

(ii)

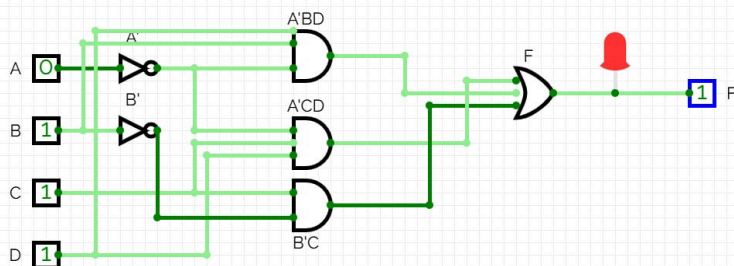

Input				Output
A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

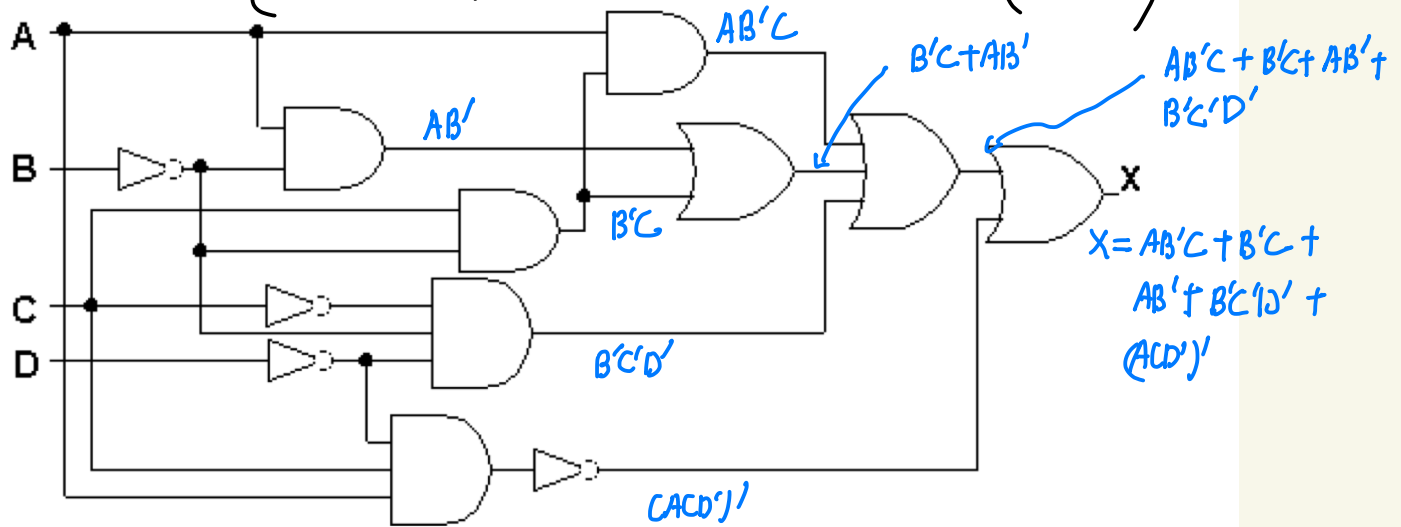5. (i) Identify the Boolean expression for the given logic diagram and obtain the truth table.



(ii) (Simplify) the identified expression using the Boolean rules, laws and theorems (Draw the truth table) for the simplified Boolean expression (Construct the circuit) for the simplified expression.

5) (i)  $X = AB'C + B'C + AB' + B'C'D' + (ACD')'$

[illegible]



$$F = A' + B' + C' + D$$

$$(ii) \quad X = AB'C + B'C + AB' + B'C'D' + (ACD')'$$

$$X = B'C(A' + 1) + AB' + B'C'D' + (A' + C' + D')$$

$$= B'C + AB' + B'C'D' + A' + C' + D$$

$$= B'C + AB' + C'(B'D' + 1) + A' + D$$

$$= B'C + AB' + C' + A' + D$$

$$= B'C + C' + \underline{A'} + \underline{AB'} + D$$

$$A + A'B = A + B$$

$$= B'C + C' + A' + B' + D$$

$$= B'(C' + 1) + C' + A' + D$$

$$= B' + C' + A' + D$$

$$= A' + B' + C' + D$$

Input				Output			
A	B	C	D	A'	B'	C'	X
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	1
0	0	1	0	1	1	0	1
0	0	1	1	1	1	0	1
0	1	0	0	1	0	1	1
0	1	0	1	1	0	1	1
0	1	1	0	1	0	0	1
0	1	1	1	1	0	0	1
1	0	0	0	0	1	1	1
1	0	0	1	0	1	1	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	1
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	1
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1

